



**END SEMESTER ASSESSMENT (ESA) B.TECH.
(CSE) III SEMESTER**

**UE20CS206 – DIGITAL DESIGN & COMPUTER
ORGANIZATION LABORATORY**

**PROJECT REPORT
ON
“4 Bit Up /Down Counter”**

SUBMITTED BY

NAME :

- 1) Shuvam Bose**
- 2) Siddhant Pathak**
- 3) Suhas TJ**
- 4) Suraj B Alagawadi**

AUGUST – DECEMBER 2021

**DEPARTMENT OF COMPUTER SCIENCE &
ENGINEERING**

**ELECTRONIC CITY CAMPUS,
BENGALURU – 560100, KARNATAKA, INDIA**

TABLE OF CONTENTS		
S1.No	TOPIC	PAGE No
1.	ABSTRACT OF THE PROJECT	1
2.	CIRCUIT DIAGRAM	2
3.	MAIN VERILOG CODE	4
4.	TEST BENCH FILE	5
5.	SCREEN SHOTS OF THE OUTPUT	6

ABSTRACT OF THE PROJECT:


A simple 4-bit up-down counter project made using Icarus Verilog as a part of the Digital Design and Computer Organization Laboratory at PES University.

We have designed an Iverilog program constructing a 4 Bit Up/Down counter which portrays the importance of counters in the calculation process of ALU.

Counters are used in many different applications. Some count up from zero and provide a change in state of output upon reaching a predetermined value (Up counter); others count down from a pre-set value to zero to provide an output state change (Down counter).

However, some counters can operate in both up and down count mode, depending on the state of an up/down count mode input pin. They can be reversed at any point within their count sequence.

CIRCUIT DIAGRAM:

 

4 Bit Up/Down Counters circuit Diagram using Flip flops.

MAIN VERILOG CODE:

```
module up_counter(input clock, reset, output[3:0] counter);
    reg [3:0] counter_up;                // Initialise register
    //counter_up to find up counter states
    always @(posedge clock or posedge reset) // Postive edge
    //triggered circuit
    begin
        if(reset)
        begin
            counter_up = 4'd0;           // If reset==1, set
            //counter to 0000
            end
        else
        begin
            counter_up = counter_up + 4'd1; // Else, add 0001
            //to counter
            end
        end
        assign counter = counter_up;      // Return new value
    //of counter
endmodule

module down_counter(input clock, reset, output [3:0] counter);
    reg [3:0] counter_down;              // Initialise register
    //counter_down to find down counter states    always
    @(posedge clock or posedge reset)      // Postive edge
    //triggered circuit
    begin
        if(reset)
        begin
            counter_down = 4'hf;          // If reset==1, set counter
            //to 1111
            end
        else
        begin
            counter_down = counter_down - 4'd1; // Else, subtract
            //0001 from counter
            end
        end
    end
```

```
        assign counter = counter_down;
    // Return new value of counter
endmodule
```

TEST BENCH FILE:

```
module counter_tb();
    reg clock, reset;
    wire [3:0] counter_1,counter_2;

    up_counter up(clock, reset, counter_1);
    down_counter down(clock, reset, counter_2);

    initial
    begin
        reset = 1;
        #0
        reset = 0;
    end


    initial
    begin
        $monitor($time,"clock=%dreset=%d
counter_1[0]=%h",clock,reset,counter_1);
    end

    initial
    begin
        clock=0;
        repeat(100)          #1
        clock=~clock;


    end
    initial
    begin
        $dumpfile("counter_tb.vcd");
        $dumpvars(0,counter_tb);
    end
endmodule
```

SCREEN SHOT OF THE OUTPUT:

Down counter gtkwave

 

Up counter gtkwave

 

VVP output:

cmd Command Prompt

```
C:\SIDDHANT\PATHAK\iverilog\bin>vvp test
VCD info: dumpfile counter_tb.vcd opened for output.
 0 clock=0 reset=0 counter_1[0]=0
 1 clock=1 reset=0 counter_1[0]=1
 2 clock=0 reset=0 counter_1[0]=1
 3 clock=1 reset=0 counter_1[0]=2
 4 clock=0 reset=0 counter_1[0]=2
 5 clock=1 reset=0 counter_1[0]=3
 6 clock=0 reset=0 counter_1[0]=3
 7 clock=1 reset=0 counter_1[0]=4
 8 clock=0 reset=0 counter_1[0]=4
 9 clock=1 reset=0 counter_1[0]=5
10 clock=0 reset=0 counter_1[0]=5
11 clock=1 reset=0 counter_1[0]=6
12 clock=0 reset=0 counter_1[0]=6
13 clock=1 reset=0 counter_1[0]=7
14 clock=0 reset=0 counter_1[0]=7
15 clock=1 reset=0 counter_1[0]=8
16 clock=0 reset=0 counter_1[0]=8
17 clock=1 reset=0 counter_1[0]=9
18 clock=0 reset=0 counter_1[0]=9
19 clock=1 reset=0 counter_1[0]=a
20 clock=0 reset=0 counter_1[0]=a
21 clock=1 reset=0 counter_1[0]=b
22 clock=0 reset=0 counter_1[0]=b
23 clock=1 reset=0 counter_1[0]=c
24 clock=0 reset=0 counter_1[0]=c
25 clock=1 reset=0 counter_1[0]=d
26 clock=0 reset=0 counter_1[0]=d
27 clock=1 reset=0 counter_1[0]=e
28 clock=0 reset=0 counter_1[0]=e
29 clock=1 reset=0 counter_1[0]=f
30 clock=0 reset=0 counter_1[0]=f
31 clock=1 reset=0 counter_1[0]=0
32 clock=0 reset=0 counter_1[0]=0
33 clock=1 reset=0 counter_1[0]=1
34 clock=0 reset=0 counter_1[0]=1
35 clock=1 reset=0 counter_1[0]=2
36 clock=0 reset=0 counter_1[0]=2
37 clock=1 reset=0 counter_1[0]=3
38 clock=0 reset=0 counter_1[0]=3
39 clock=1 reset=0 counter_1[0]=4
40 clock=0 reset=0 counter_1[0]=4
41 clock=1 reset=0 counter_1[0]=5
42 clock=0 reset=0 counter_1[0]=5
43 clock=1 reset=0 counter_1[0]=6
44 clock=0 reset=0 counter_1[0]=6
45 clock=1 reset=0 counter_1[0]=7
46 clock=0 reset=0 counter_1[0]=7
47 clock=1 reset=0 counter_1[0]=8
48 clock=0 reset=0 counter_1[0]=8
49 clock=1 reset=0 counter_1[0]=9
50 clock=0 reset=0 counter_1[0]=9
51 clock=1 reset=0 counter_1[0]=a
```

cmd Select Command Prompt

```
51 clock=1 reset=0 counter_1[0]=a
52 clock=0 reset=0 counter_1[0]=a
53 clock=1 reset=0 counter_1[0]=b
54 clock=0 reset=0 counter_1[0]=b
55 clock=1 reset=0 counter_1[0]=c
56 clock=0 reset=0 counter_1[0]=c
57 clock=1 reset=0 counter_1[0]=d
58 clock=0 reset=0 counter_1[0]=d
59 clock=1 reset=0 counter_1[0]=e
60 clock=0 reset=0 counter_1[0]=e
61 clock=1 reset=0 counter_1[0]=f
62 clock=0 reset=0 counter_1[0]=f
63 clock=1 reset=0 counter_1[0]=0
64 clock=0 reset=0 counter_1[0]=0
65 clock=1 reset=0 counter_1[0]=1
66 clock=0 reset=0 counter_1[0]=1
67 clock=1 reset=0 counter_1[0]=2
68 clock=0 reset=0 counter_1[0]=2
69 clock=1 reset=0 counter_1[0]=3
70 clock=0 reset=0 counter_1[0]=3
71 clock=1 reset=0 counter_1[0]=4
72 clock=0 reset=0 counter_1[0]=4
73 clock=1 reset=0 counter_1[0]=5
74 clock=0 reset=0 counter_1[0]=5
75 clock=1 reset=0 counter_1[0]=6
76 clock=0 reset=0 counter_1[0]=6
77 clock=1 reset=0 counter_1[0]=7
78 clock=0 reset=0 counter_1[0]=7
79 clock=1 reset=0 counter_1[0]=8
80 clock=0 reset=0 counter_1[0]=8
81 clock=1 reset=0 counter_1[0]=9
82 clock=0 reset=0 counter_1[0]=9
83 clock=1 reset=0 counter_1[0]=a
84 clock=0 reset=0 counter_1[0]=a
85 clock=1 reset=0 counter_1[0]=b
86 clock=0 reset=0 counter_1[0]=b
87 clock=1 reset=0 counter_1[0]=c
88 clock=0 reset=0 counter_1[0]=c
89 clock=1 reset=0 counter_1[0]=d
90 clock=0 reset=0 counter_1[0]=d
91 clock=1 reset=0 counter_1[0]=e
92 clock=0 reset=0 counter_1[0]=e
93 clock=1 reset=0 counter_1[0]=f
94 clock=0 reset=0 counter_1[0]=f
95 clock=1 reset=0 counter_1[0]=0
96 clock=0 reset=0 counter_1[0]=0
97 clock=1 reset=0 counter_1[0]=1
98 clock=0 reset=0 counter_1[0]=1
99 clock=1 reset=0 counter_1[0]=2
100 clock=0 reset=0 counter_1[0]=2
```

C:\SIDDHANT\PATHAK\iverilog\bin>